 


COEN 21 Lab 5 Report

1)

- a.)  $X=4'b0000$  (Hex: 0) &  $Y=4'b0000$  (Hex: 0)
- b.)  $X=4'b0100$  (Hex: 4) &  $Y=4'b0100$  (Hex: 4)
- c.)  $X=4'b1100$  (Hex = 9) &  $Y=4'b1100$  (Hex: 7)
- d.)  $X=4'b1100$  (Hex = C) &  $Y=4'b1000$  (Hex: A)

2)



3)

The Initial testing of the circuit went smoothly, and there were no errors in our Verilog code to cause any.

4) No, we would not be able to find a difference from the output, because the bits would be added normally since they are the same as their original values before swapping.

5)

- a) It is showing incorrect results at S1 and S0 (b1 and b0) (the values are swapped).
- b) What is wrong is that the wires for S1 and S0 are connected to the incorrect outputs.



- c) A test that might help to prove my hypothesis is to set the Inputs X and Y to 0100 and 0001 respectively, and the correct outputs would be 0101, while the incorrect output would be 0110.

### Schematics, Verilog, and Waveforms

```

1  module myfulladd(A,B,CIN,SOUT,COUT);
2      input A,B,CIN;
3      output SOUT,COUT;
4
5      assign SOUT=A ^ B ^ CIN;
6      assign COUT=(A & B)|(B & CIN)|(A & CIN);
7  endmodule
8
9  module myadder4(X,Y,c0,s,v,c4);
10     input c0;
11     input [3:0]X,Y;
12     output [3:0]s;
13     output v,c4;
14     wire [2:0]c;
15
16     myfulladd(X[0],Y[0],c0,s[0],c[0]);
17     myfulladd(X[1],Y[1],c[0],s[1],c[1]);
18     myfulladd(X[2],Y[2],c[1],s[2],c[2]);
19     myfulladd(X[3],Y[3],c[2],s[3],c4);
20     assign v=c4^c[2];
21 endmodule

```

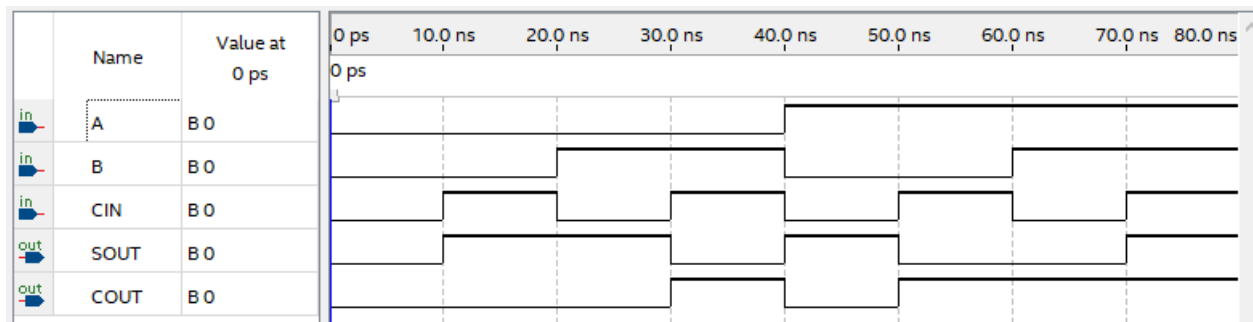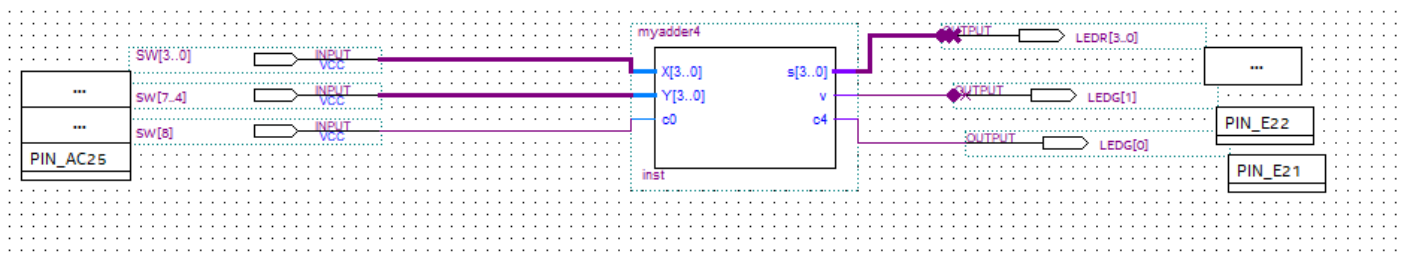

### Truth Table Result

X	Y	C0	S	V	C4
0	0	0	0000	0	0
0	0	1	0001	0	0
1	0	0	0001	0	0

0	1	0	0001	0	0
2	0	0	0010	0	0
4	3	0	0111	0	0
4	4	0	1000	1	0
9	6	0	1111	0	0
9	7	0	0000	0	1
C	A	0	0110	1	1
E	A	0	1000	0	1
E	A	1	1001	0	1