

Santa Clara University	COEN 21 – Winter 2022	Name: <u>TUSHAR SHRESTHA</u>
Homework #1		
Please scan and upload your completed homework on Camino   Due Date: 1/7/2022		

Draw the (1) truth table; (2) Boolean expressions, and (3) logic gates symbol/schematic for each of the following:

- 2-input AND gate
- 2-input OR gate
- 2-input NAND gate
- 2-input NOR gate
- 2-input Exclusive-OR gate
- 2-input Exclusive-NOR gate
- NOT gate

### • 2-input AND GATE


1) Truth table

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

2) Boolean Expression

$$z = x \cdot y = xy$$

3) Logic Gates Symbol/Schematic

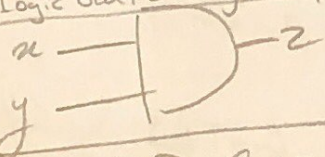

### • 2-input OR GATE


1) Truth TABLE

x	y	z
0	0	0
1	0	1
0	1	1
1	1	1

2) Boolean Expression

$$z = x + y$$

Logic Gates Symbol/Schematic

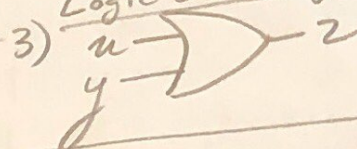

### • 2-input NAND GATE


1) Truth TABLE

x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

2) Boolean Expression

$$z = \overline{x \cdot y}$$

3) Logic gates Symbol/Schematic

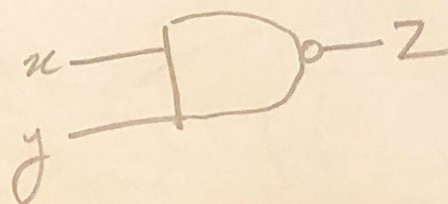

## 2 input - NOR GATE


### 1) TRUTH TABLE

x	y	z
0	0	1
0	1	0
1	0	0
1	1	0

### 2) Boolean Expression

$$z = \overline{x + y}$$

### 3) Logic GATES Symbol/Schema

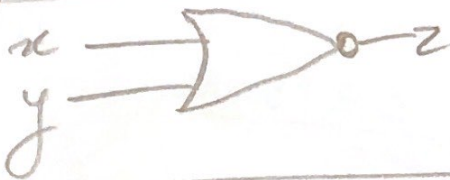

## 2-input-exclusive-NOR GATE

### 1) TRUTH TABLE

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0

### 2) Boolean Expression

$$z = x \oplus y$$

### 3) Logic GATES Symbol/Schema



## 2 input - exclusive-NOR GATE


### 1) TRUTH TABLE

x	y	z
0	0	1
0	1	0
1	0	0
1	1	1

### 2) Boolean Expression

$$z = \overline{x \oplus y}$$

### 3) Logic GATES Symbol/Schema

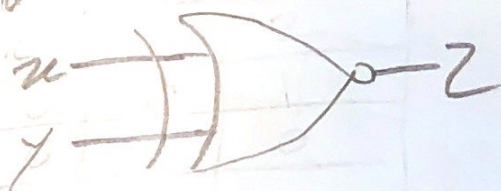

## NOT GATE

### 1) TRUTH TABLE

x	y
0	1
1	0

### 2) Boolean Expression

$$y = \overline{x}$$

### 3) Logic GATES Symbol/Schema

