

Santa Clara University	COEN 21 – Winter 2022	Name:
Homework #3 (10 points)		
Please scan and upload your completed homework on Camino Due Date: 1/21/2022		


#1: An example of gate sharing is given below Two functions, f_1 and f_2 , of the same variables are to be implemented. The minimum-cost implementations for these functions are obtained as shown in parts (a) and (b) of the figure. This results in the expressions

$$f_1 = x_1\bar{x}_3 + \bar{x}_1x_3 + x_2\bar{x}_3x_4$$


$$f_2 = x_1\bar{x}_3 + \bar{x}_1x_3 + x_2x_3x_4$$

The cost of f_1 is four gates and 10 inputs, for a total of 14. The cost of f_2 is the same. Thus the total cost is 28 if both functions are implemented by separate circuits. A less-expensive realization is possible if the two circuits are combined into a single circuit with two outputs. Because the first two product terms are identical in both expressions,

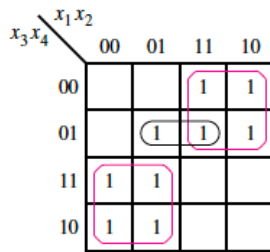DRAW the combined circuit with two outputs.



(a) Function f_1

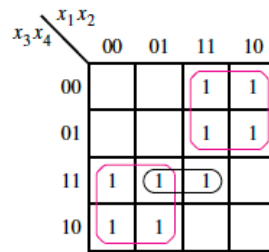

(b) Function f_2

SOLUTION

#2: For the following function $F(x, y, z) = \sum m(1, 2, 3, 5, 7)$

- Draw the Karnaugh map for the above function
- Find the optimal SOP equation for the above function.
- Draw the logic circuit for the above function.

SOLUTION

#3 Simplify $F(w, x, y, z) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

- Draw the Karnaugh map for the above function
- Write the algebraic equation from the Karnaugh map

SOLUTION